



Cyprus  
University of  
Technology

## EEN320 - Power Systems I (Συστήματα Ισχύος Ι)

Part 5: The transmission line

Dr Petros Aristidou

Department of Electrical Engineering, Computer Engineering & Informatics

Last updated: March 21, 2020


After this part of the lecture and additional reading, you should be able to . . .

- ① . . . name the main components of an overhead line and describe their functionality;
- ② . . . understand how to derive the  $\Pi$ -equivalent circuit of a transmission line;
- ③ . . . determine the parameters of the  $\Pi$ -equivalent circuit of a transmission line from its concentrated parameters;
- ④ . . . explain how and under which conditions or assumptions the  $\Pi$ -equivalent circuit can be further simplified.

# Outline


- 1 **Physical relevance of power lines**
- 2 **Structure of overhead lines**
  - Conductors
  - Support structures
  - Insulators
  - Shield wires
- 3 **Derivation of lumped inductor and capacitor values**
  - Inductance
  - Capacitance
- 4 **Overhead line parameters**
  - Concentrated parameters
  - Some brief remarks on cables
- 5 **Equivalent circuits for power lines**
  - Differential equation of a power line
  - Solution of differential equation of a power line
  - $\Pi$ -equivalent circuit
  - Model simplifications and their validity

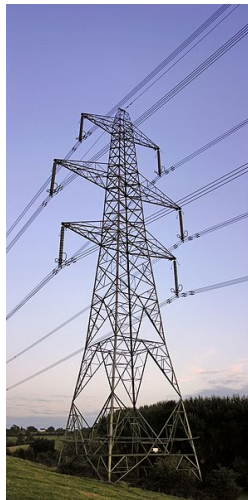- Task: Transport electricity
  - 2 main types:
    - Overhead line (OL)
    - Cable
  - OLs and cables possess different structure and operational properties
  - At same voltage level, costs for cables approx. 10-20 times than costs of OLs
- OLs economically more viable option



Overhead power line in Gloucestershire, England ©Yummifruitbat
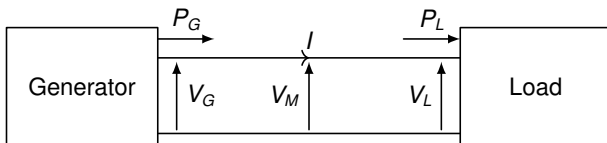
## 1 Recap: Motivation for high voltage transmission (1)



Simplified DC transmission system

- Line is resistive  $\rightarrow$  voltage drop across line  $\rightarrow V_G > V_M > V_L$
- Average power transmitted over line:  $P_{trans} = V_M I$   
( $V_M$  is voltage at middle of line length)

- Denote total line resistance by  $R \rightarrow$  line losses given by

$$P_{loss} = RI^2 = R \left( \frac{P_{trans}}{V_M} \right)^2$$

- Ratio of power losses to transmitted power


$$\frac{P_{loss}}{P_{trans}} = R \frac{P_{trans}}{V_M^2}$$

- Ratio of power losses to transmitted power

$$\frac{P_{loss}}{P_{trans}} = R \frac{P_{trans}}{V_M^2}$$

- Power losses inversely proportional to square of operational voltage  $V_M^2$
- Power lines usually operated at high voltage
- However, higher voltage means higher insulation of components
- Higher costs

# 1 Costs vs. transmission voltage

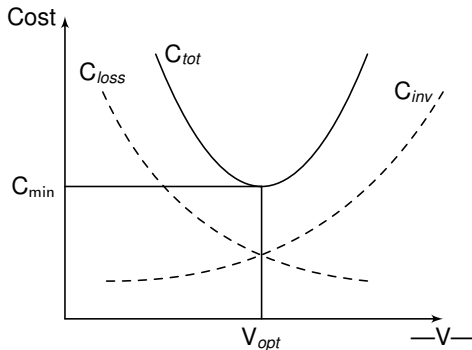


- Total costs  $C_{tot} = C_{loss} + C_{inv}$
- Minimum costs  $C_{min} \rightarrow$  economically optimal operating voltage
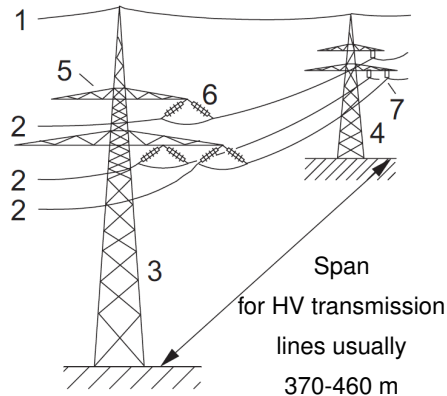
## 2 Structure of overhead lines - Main components

An overhead line consists of


- Conductors (2)
- Support structures
  - Towers (and poles) (3,4)
  - Traverse (5)
- Shield wires (1)
- Insulators (6,7)
  - Strain-type insulator (6)
  - Suspension-type insulator (7)



Source: K. Heuck et al., "Elektrische Energieversorgung", Springer, 2013




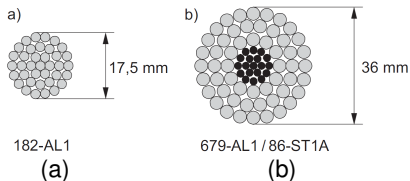- Aluminium is most common conductor metal
- Copper also used, but less frequently as heavier and more expensive
- Mechanical strain acting on conductors limits span between towers (line sag)
- For short lines, conductors of pure aluminium strands may be used (Figure (a))
- For longer lines, conductors are *reinforced* with central steel strands (Figure (b))



Source: K. Heuck et al., "Elektrische Energieversorgung", Springer, 2013

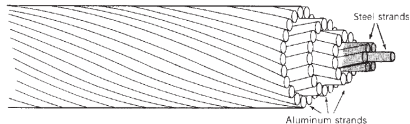Strands are usually twisted to reduce Eddy currents



Source: J. Duncan Glover et al., "Power System Analysis & Design", Cengage Learning, 2008


## 2.1 Conductors - Types

- Common types of conductors
  - Aluminium conductor steel-reinforced (ACSR)
  - All-Aluminium conductor (AAC)
  - All-Aluminium alloy conductor (AAAC)
  - Aluminium conductor composite reinforced (ACCR)
  - Aluminium conductor composite core (ACCC)

- Conductors labeled based on cross section (in  $\text{mm}^2$ ) of aluminium and core strand

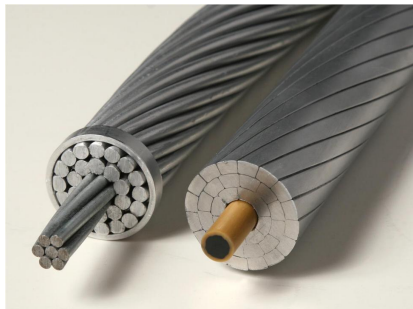Example: 243-AL1/39-ST1A

(code after AL and ST denotes finishing properties of AL and ST)




©Dave Bryant

Standard round-wire ACSR (left) and ACCC with trapezoidal wires (right)

ACCR and ACCC use carbon and glass fiber core → up to 10 times lower thermal expansion coefficient than steel → can use more aluminium → reduced line losses

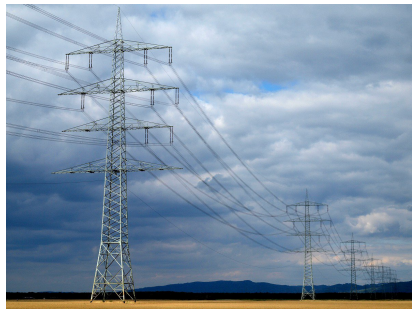
- Each phase of a three-phase transmission line consists of one or more conductors
- More than one conductor/phase → bundled conductor
- Advantages:
  - Smaller series resistance
  - Reduced electric field strength at conductor surface → reduced Corona effect
- Transmission line may also consist of several three-phase systems in parallel



©Kreuzschnabel

Triple-circuit 400 kV overhead line with  
4 conductors per phase

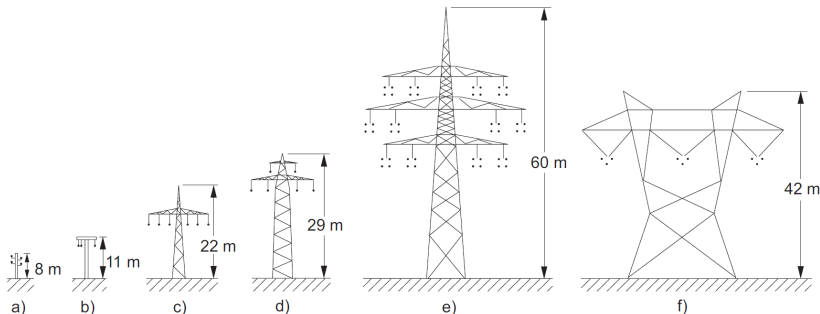
## 2.2 Support structures - Towers and poles




Source: K. Heuck et al., "Elektrische Energieversorgung", Springer, 2013

- Large variety of support structures
- Poles made of wood or concrete [a) and b)] used for voltages  $\leq 110$  kV
- Self-supporting lattice steel towers [c) - f)] used for voltages  $\geq 110$  kV

- Need to insulate "live" conductors from tower
- Pin-type insulators (for lower voltages < 60 kV); material: porcelain; Figure (a)
- Suspension-type insulators (for voltages > 60 kV)
  - Suspension disc insulator; material: glass; Figure (b)
  - Long-rod insulator; material: porcelain; Figure (c)  
(Strain-type insulator some times also used)
- To prevent sparkovers, insulators need to be sufficiently long (approx. 1.5 cm/kV) and possess appropriate shape to minimise leakage currents

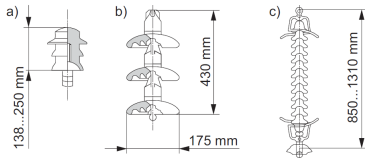


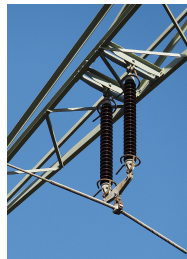Source: K. Heuck et al., "Elektrische Energieversorgung", Springer, 2013




110 kV double long-rod suspension string  
©Kreuzschnabel

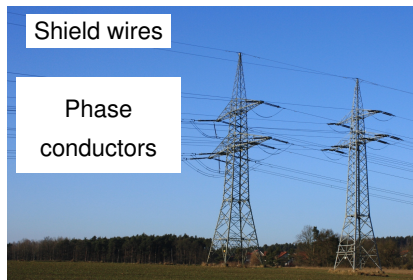- Shield wires located above phase conductors to provide protection against lightning
- Shield wires are grounded to tower
- They also serves as parallel path with Earth for fault currents
- Predominantly used above 110 kV
- Much smaller cross section than phase conductors
- Modern shield wires contain optical fibres for communication/control
- Usually, 1-2 shield wires used



©Kreuzschnabel

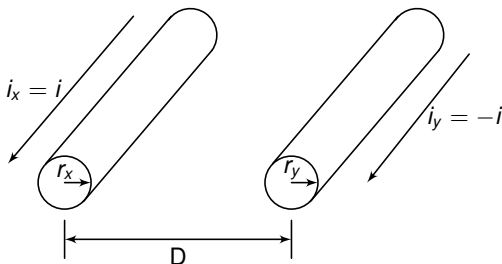


- $r_x, r_y$ : radius of cylindrical conductors
- $D$ : spacing between conductors
- $i$ : current flowing in conductors
- **Assumptions:** Conductors are of infinitely length, non-magnetic ( $\mu = \mu_0$ )<sup>1</sup> and have uniform current density (skin-effect neglected)

---

<sup>1</sup>  $\mu_0$  is vacuum permeability constant
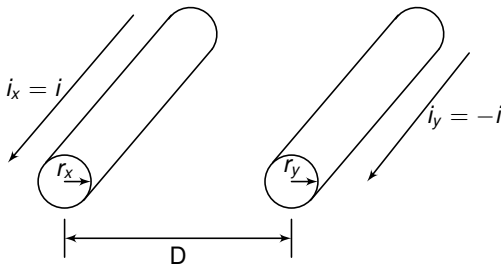
## 3.1 Inductance of a single-phase two-wire line (2)




- Inductance of one conductor  $k = \{x, y\}$

$$L'_k = \frac{\mu_0}{2\pi} \ln \left( \frac{D}{r'_k} \right) = 2 \cdot 10^{-7} \ln \left( \frac{D}{r'_k} \right) [\text{H/m}] \quad r'_k = r_k e^{-\frac{1}{4}} \approx 0.778r$$

$$\mu_0 = 4\pi \cdot 10^{-7}$$



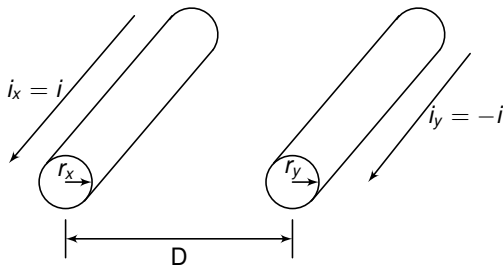
### 3.1 Inductance of a single-phase two-wire line (3)



- Total inductance of single-phase two-wire line

$$\begin{aligned} L' &= L'_x + L'_y = 2 \cdot 10^{-7} \left( \ln \left( \frac{D}{r'_x} \right) + \ln \left( \frac{D}{r'_y} \right) \right) \\ &= 2 \cdot 10^{-7} \ln \left( \frac{D^2}{r'_x r'_y} \right) = 4 \cdot 10^{-7} \ln \left( \frac{D}{\sqrt{r'_x r'_y}} \right) \text{ [H/m]} \end{aligned}$$

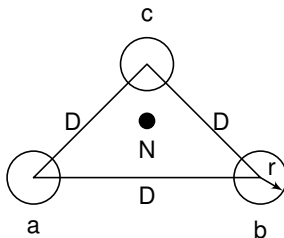- Identical conductors ( $r_x = r_y$ ):  $L' = 4 \cdot 10^{-7} \ln \left( \frac{D}{r'} \right) \text{ [H/m]}$



- Assumptions: balanced phase currents, equidistant spacing  $D$ , identical conductor radii  $r$
- Line-neutral inductances of three-phase three-wire line

$$L' = L'_a = L'_b = L'_c = 2 \cdot 10^{-7} \ln \left( \frac{D}{r'} \right) [\text{H/m}]$$

- This is half the inductance of a single-phase two-wire line!
- Inductances balanced  $\rightarrow$  can use single-phase equivalent circuit for network calculations


### 3.1 Inductance of a three-phase three-wire line - Transposition of conductors

- In practice, conductors rarely spaced in equidistant manner
- Inductances become unbalanced ( $L_a \neq L_b \neq L_c$ ) → this causes unbalanced voltage drops even if currents are balanced!
- Practical remedy: restore balance by exchanging conductor positions along line (e.g. at substations)
- This is called *transposition*
- For transposed line with equivalent spacing  $D_{eq} = \sqrt[3]{D_{12} D_{23} D_{31}}$

$$L' = L'_a = L'_b = L'_c = 2 \cdot 10^{-7} \ln \left( \frac{D_{eq}}{D_S} \right) \text{ [H/m]}$$

$D_S$  ... geometric mean radius (GMR) for stranded conductors

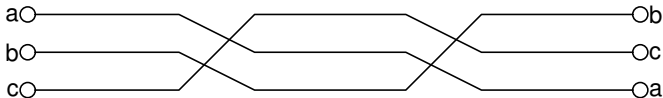$D_S = r'$  for solid cylindrical conductors




### 3.1 Example: Determine inductance of a three-phase three-wire line

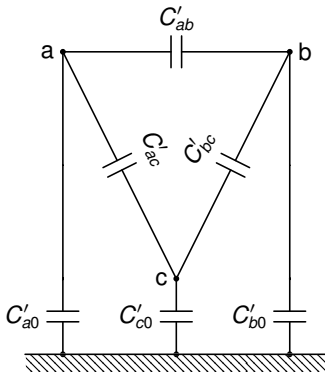**Task.** A completely transposed 50-Hz three-phase line has flat horizontal phase spacing with 10m between adjacent conductors. The geometric mean radius (GMR) of the conductors is 0.0159m. The line length is  $\ell = 200\text{km}$ . Determine the inductance in H and the inductive reactance in  $\Omega$ .


**Solution.** (On board)

- Line capacitance can be obtained in similar fashion to inductances
- Need to consider interaction of electric fields between conductors *and* between individual conductors and earth
- This can be modelled via coupling and earth capacitances



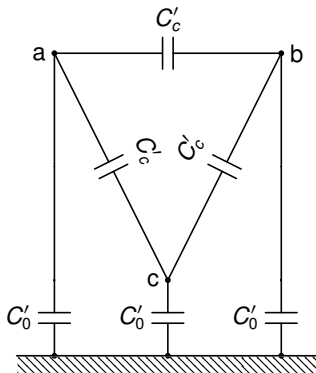
## 3.2 Capacitance - Balanced three-phase three-wire line (1)

- Assume balanced line (e.g. via transposition)
- Then,  $C'_0 = C'_{a0} = C'_{b0} = C'_{c0}$  and  $C'_c = C'_{ab} = C'_{ac} = C'_{bc}$
- Coupling conductors  $C'_c$  form  $\Delta$ -connection



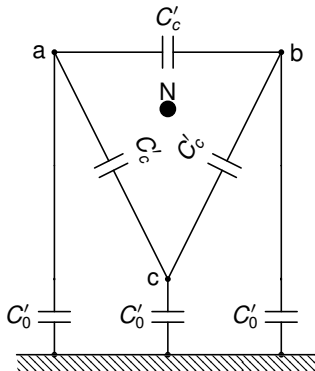
## 3.2 Capacitance - Balanced three-phase three-wire line (2)

- Assume balanced line (e.g. via transposition)
- Then,  $C'_0 = C'_{a0} = C'_{b0} = C'_{c0}$  and  $C'_c = C'_{ab} = C'_{ac} = C'_{bc}$
- Coupling conductors  $C'_c$  form  $\Delta$ -connection
- Introduce *fictitious* neutral point N


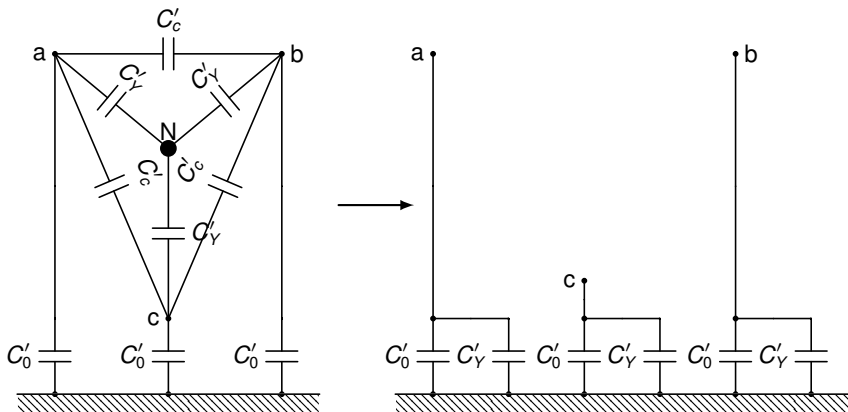
## 3.2 Capacitance - Balanced three-phase three-wire line (3)

- Balanced conditions  $\rightarrow$  sum of currents at N equal zero  $\rightarrow$  N has same potential as ground
- Parallel connection of coupling and earth capacitances  $C'_Y = 3C'_c$






- Balanced conditions  $\rightarrow$  sum of currents at N equal zero  $\rightarrow$  N has same potential as ground
- Parallel connection of coupling and earth capacitances  $C' = C'_Y + C'_0$


$$C' = \frac{2\pi\epsilon_0}{\ln\left(\frac{D_{eq}}{r}\right)} \text{ [F/m]} \quad \epsilon_0 \dots \text{vacuum permittivity}$$

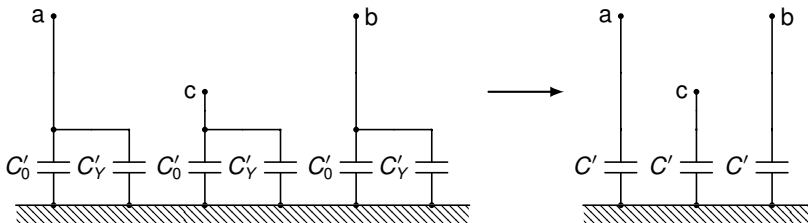- Typical value for overhead lines  $C' \approx 10 \text{ nF/km}$



Note: similar calculations applicable to conductor bundles
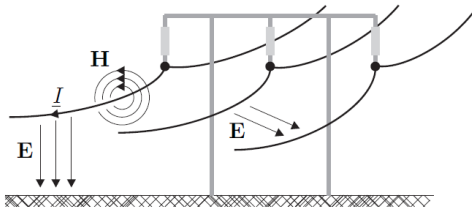
### Magnetic and electric fields of conducting power line




E... electric field

H... magnetic field

©G. Anderson


- Each power line has characteristic line parameters
- Parameters dependent on line geometry and material
- Parameters often indicated in [unit]/km and by giving the line length  $\ell$

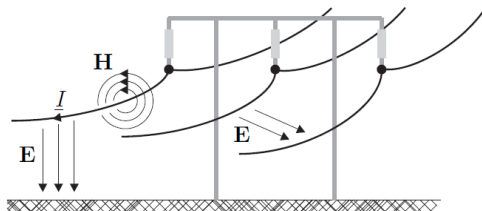Magnetic and electric fields  
of conducting power line




©G. Anderson

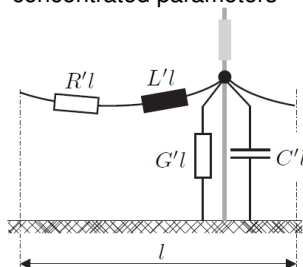Power line model with  
concentrated parameters




- Line resistance  $R'$  [ $\Omega/\text{km}$ ]  $\leftrightarrow$  Ohmic resistance of conductor
- Line inductance  $L'$  [ $\text{H}/\text{km}$ ]  $\leftrightarrow$  Magnetic field of conductor
- Capacitance  $C'$  [ $\text{F}/\text{km}$ ]  $\leftrightarrow$  Electric field of conductor
- Shunt conductance  $G'$  [ $\text{S}/\text{km}$ ]  $\leftrightarrow$  Leakage currents at insulators

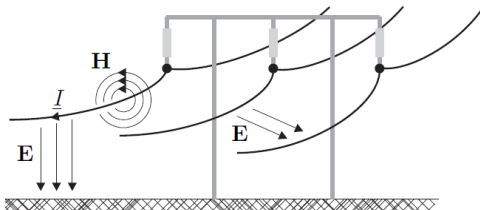Magnetic and electric fields  
of conducting power line



©G. Anderson

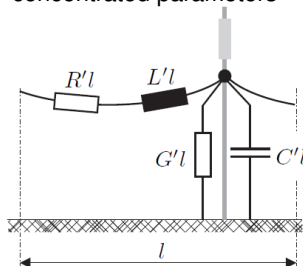Power line model with  
concentrated parameters



- For performing circuit analysis involving power lines (e.g. to determine the network conditions or design) we need to know the concentrated parameters of the lines
- Usually, concentrated parameters indicated by manufacturer

Please see the course book for a detailed derivation.

- Real conductors are not lossless!
- This can be accounted for by including a series resistance in the conductor model
- For DC current, resistance of conductor can easily be determined from its diameter, length and specific conductivity
- For AC current, in addition the *skin effect* needs to be considered when determining the resistance of a conductor
- Skin-effect: current not distributed homogeneously over conductor diameter, but concentrated towards conductor boundaries
- Current density increases towards conductor boundaries
- Effective diameter of conductor is reduced and, hence, ohmic resistance is increased compared to DC resistance (typically by a few percent)

## 4.1 Resistance - Calculation

- For steel-reinforced aluminium conductors (ACSR), AC resistance is approximately same as DC resistance
- Reason: Skin-effect → reduced AC current in steel strands → increase in AC resistance by skin-effect comparable to higher DC current in steel strands
- Conductor losses result in heat dissipation → maximum conductor current limited, as long-term high temperatures ( $> 80^{\circ}$ ) decrease mechanical strength of conductor material → line sags
- Line resistance operating at temperature of  $\vartheta^{\circ}$  can be calculated via

$$R' = R'_{20}(1 + \alpha(\vartheta - 20^{\circ}\text{C})) \text{ [R/m]}$$

$$R'_{20} = \frac{\rho_{20}}{A} \text{ resistance of conductor at } 20^{\circ}\text{C}$$

$\rho_{20}$ ... specific resistance of conductor material at  $20^{\circ}\text{C}$

$A$ ... effective conductor area

- For practical conductors, resistance values obtained via measurements

- Also, losses due to insulator leakage currents and corona
- Corona: high value of electric field strength at conductor surface causes air to become electrically ionised and to conduct
- Corona losses dependent on meteorological conditions (rain; humidity) and conductor surface irregularities
- For overhead lines, conductance  $G'$  can only be estimated from measurements, while it can be determined experimentally for cables
- Usually, conductance is very small and therefore most often neglected in power system studies

## 4.2 Cables vs. overhead lines

- Cables mostly used at low voltage levels ( $<110$  kV)
- Often installed underground
- Physical characteristics of cables fundamentally different from overhead transmission lines (OHLs)!
- Main reasons:
  - Distance between conductors as well as between conductors and earth much smaller in cables than in OHLs
  - Conductors in cables typically surrounded by other metallic materials, e.g. skin
  - Insulation material of OHLs is air, while in cables materials such as paper, oil or  $\text{SF}_6$  are used
- Consequences:
  - Inductance of OHLs usually higher as that of cables
  - Capacitance of cables usually much higher as that of OHLs



- Typical values for parameters of OHLs at 50 Hz


Rated voltage in kV	230	345	500	765
$R'$ [ $\Omega/\text{km}$ ]	0.050	0.037	0.028	0.012
$X'_L = \omega L'$ [ $\Omega/\text{km}$ ]	0.407	0.306	0.271	0.274
$Y'_C = \omega C'$ [ $\mu\text{S}/\text{km}$ ]	2.764	3.765	4.333	4.148

- Typical values for parameters of cables at 50 Hz

Rated voltage in kV	115	230	500
$R'$ [ $\Omega/\text{km}$ ]	0.059	0.028	0.013
$X'_L = \omega L'$ [ $\Omega/\text{km}$ ]	0.252	0.282	0.205
$Y'_C = \omega C'$ [ $\mu\text{S}/\text{km}$ ]	192.0	204.7	80.4


- Being able to describe the behaviour of a power systems by a mathematical model is a fundamental prerequisite for network planning and operation
  - We will derive a model of a power line that is valid under *stationary* (or steady-state) conditions
  - Note: A real power system is never exactly in steady-state due to continuous variations of load and generation
  - However, under normal conditions this variations are of small magnitude compared to overall power flows in network
  - Also, normal load patterns change over fairly long period (several tens of minutes)
- Steady-state model suitable for describing nominal network operating conditions

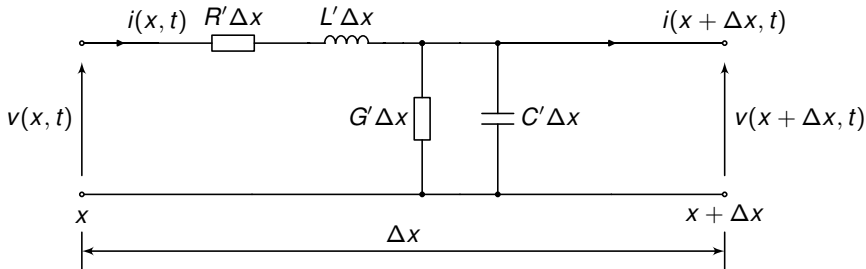Section of length  $\Delta x$  of homogeneous power line



- Line parameters  $R'$ ,  $L'$ ,  $G'$  and  $C'$  are not lumped, but (uniformly) distributed along length of line;  $\Delta x$  denotes a small distance
- Propagation of current  $i(t, x)$  and voltage  $v(t, x)$  across that line segment is not instantaneous
- Propagation can be described by a partial-differential equation (i.e. propagation depends on time  $t$  and location  $x$ )

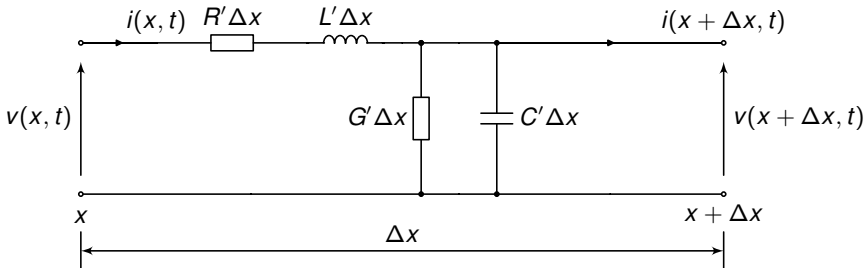Section of length  $\Delta x$  of homogeneous power line




- From KVL

$$v(x + \Delta x, t) = v(x, t) - R' \Delta x i(x, t) - L' \Delta x \frac{\partial i(x, t)}{\partial t}$$

- From KCL

$$i(x + \Delta x, t) = i(x, t) - G' \Delta x v(x + \Delta x, t) - C' \Delta x \frac{\partial v(x + \Delta x, t)}{\partial t}$$

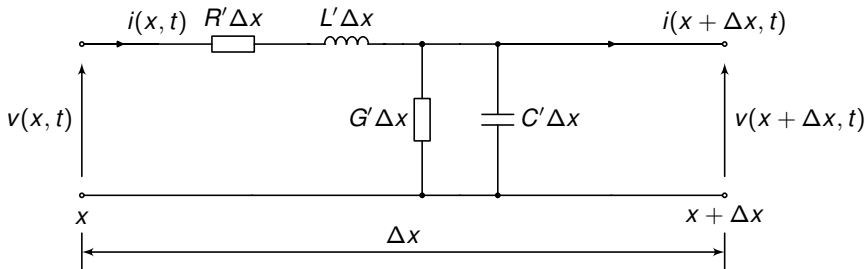
Section of length  $\Delta x$  of homogeneous power line



- For infinitesimally small section length  $\Delta x \rightarrow 0$ , previous equations are equivalent to

$$\frac{\partial v}{\partial x} = - \left( R' + L' \frac{\partial}{\partial t} \right) i$$
$$\frac{\partial i}{\partial x} = - \left( G' + C' \frac{\partial}{\partial t} \right) v$$

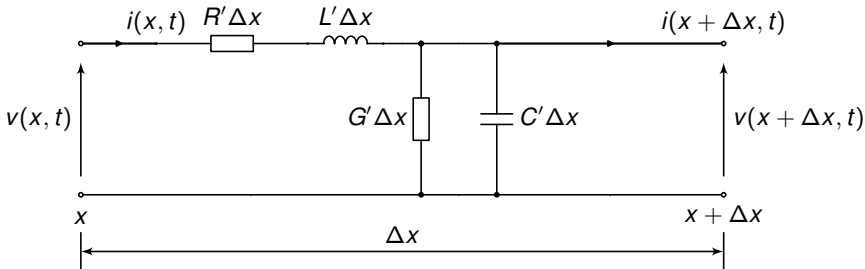Section of length  $\Delta x$  of homogeneous power line



- Decouple equations by differentiating first wrt  $x$  and second wrt  $t$  and insert resulting expressions in equations (derived by Maxwell around 1860)

$$\begin{aligned} \frac{\partial^2 v}{\partial x^2} &= R' G' v + (R' C' + L' G') \frac{\partial v}{\partial t} + L' C' \frac{\partial^2 v}{\partial t^2} \\ \frac{\partial^2 i}{\partial x^2} &= R' G' i + (R' C' + L' G') \frac{\partial i}{\partial t} + L' C' \frac{\partial^2 i}{\partial t^2} \end{aligned}$$

- In power systems, we are mostly interested in solving telegrapher's equations for special case of *sinusoidal excitation*
- For that case, voltage  $v(x, t)$  and current  $i(x, t)$  can be represented as phasors with complex amplitudes  $\underline{V}$  and  $\underline{I}$  and frequency  $\omega = 2\pi f$ :

$$u(x, t) = \Re \left( \underline{V}(x) e^{j\omega t} \right)$$

$$i(x, t) = \Re \left( \underline{I}(x) e^{j\omega t} \right)$$

- By using phasors, telegrapher's equations reduce to two linear first-order differential equations

$$\begin{aligned}\frac{d\underline{V}}{dx} &= -(R' + j\omega L')\underline{I} \\ \frac{d\underline{I}}{dx} &= -(G' + j\omega C')\underline{V}\end{aligned}$$

- Eliminating  $\underline{I}(x)$  leaves us with a linear homogeneous second-order differential equation, which is called *wave equation*

$$\boxed{\frac{d^2 \underline{V}}{dx^2} = (R' + j\omega L')(G' + j\omega C')\underline{V}}$$

- Note: introduction of phasors transforms partial differential equation in ordinary differential equation (i.e. in one variable)



- The solution of the wave equation can be computed as

$$\underline{V}(x) = \underline{V}^+ e^{-\underline{\gamma}x} + \underline{V}^- e^{\underline{\gamma}x}$$

- $\underline{V}^+$  and  $\underline{V}^-$  are integration constants
- $\underline{\gamma}$  is called *propagation constant*

$$\underline{\gamma} = \sqrt{(R' + j\omega L')(G' + j\omega C')}$$

- Writing the solution of the wave equation as a function of time, we obtain

$$v(x, t) = \Re \left( \underbrace{\underline{V}^+ e^{-\underline{\gamma}x} e^{j\omega t}}_{\text{forward travelling wave}} + \underbrace{\underline{V}^- e^{\underline{\gamma}x} e^{j\omega t}}_{\text{backward travelling wave}} \right)$$

- Forward travelling (voltage) wave moves in positive  $x$ -direction
- Backward travelling (voltage) wave moves in negative  $x$ -direction (also called *reflected wave*)
- Complex propagation constant  $\underline{\gamma}$  can be split in real and imaginary part

$$\underline{\gamma} = \alpha + j\beta$$

- $\alpha$  describes damping of (voltage) wave and is measured in Nepers per unit length <sup>2</sup>
- $\beta$  describes phase of (voltage) wave at distance  $x$  from origin and is measured in radians per unit length

---

<sup>2</sup>Np=Neper is a logarithmic unit to measure physical field quantities.

## 5.2 Solution of the wave equation - Current

- By differentiating  $\underline{V}(x)$  we obtain

$$\frac{d\underline{V}}{dx} = -\underline{\gamma}\underline{V}^+ e^{-\underline{\gamma}x} + \underline{\gamma}\underline{V}^- e^{\underline{\gamma}x}$$

and, hence,

$$\begin{aligned} \underline{I}(x) &= \frac{1}{-(R' + j\omega L')} \frac{d\underline{V}}{dx} = \frac{-\underline{\gamma}\underline{V}^+ e^{-\underline{\gamma}x} + \underline{\gamma}\underline{V}^- e^{\underline{\gamma}x}}{-(R' + j\omega L')} \\ &= \sqrt{\frac{G' + j\omega C'}{R' + j\omega L'}} (\underline{V}^+ e^{-\underline{\gamma}x} - \underline{V}^- e^{\underline{\gamma}x}) \end{aligned}$$

- Define *surge impedance* (also called characteristic impedance)

$$\underline{Z}_w = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

$$\Rightarrow \underline{I}(x) = \frac{1}{\underline{Z}_w} (\underline{V}^+ e^{-\underline{\gamma}x} - \underline{V}^- e^{\underline{\gamma}x})$$

- Boundary conditions at beginning of line ( $x = 0$ )

$$\underline{V}(0) = \underline{V}_1 \quad \underline{I}(0) = \underline{I}_1$$

- Inserting these values in solutions for  $\underline{V}(x)$  and  $\underline{I}(x)$  at  $x = 0$  yields

$$\begin{aligned}\underline{V}_1 &= \underline{V}^+ + \underline{V}^- \\ \underline{I}_1 &= \frac{\underline{V}^+ - \underline{V}^-}{\underline{Z}_w}\end{aligned}$$

- Solving for  $\underline{V}^+$  and  $\underline{V}^-$ , we obtain

$$\begin{aligned}\underline{V}^+ &= \frac{\underline{V}_1 + \underline{Z}_w \underline{I}_1}{2} \\ \underline{V}^- &= \frac{\underline{V}_1 - \underline{Z}_w \underline{I}_1}{2}\end{aligned}$$

- Substituting expressions for  $\underline{V}^+$  and  $\underline{V}^-$  in equations for  $\underline{V}(x)$  and  $\underline{I}(x)$  yields

$$\begin{aligned}\underline{V}(x) &= \left( \frac{\underline{V}_1 + \underline{Z}_W \underline{I}_1}{2} \right) e^{-\gamma x} + \left( \frac{\underline{V}_1 - \underline{Z}_W \underline{I}_1}{2} \right) e^{\gamma x} \\ &= \left( \frac{e^{\gamma x} + e^{-\gamma x}}{2} \right) \underline{V}_1 - \underline{Z}_W \underline{I}_1 \left( \frac{e^{\gamma x} - e^{-\gamma x}}{2} \right)\end{aligned}$$

$$\begin{aligned}\underline{I}(x) &= \left( \frac{\underline{V}_1 + \underline{Z}_W \underline{I}_1}{2 \underline{Z}_W} \right) e^{-\gamma x} - \left( \frac{\underline{V}_1 - \underline{Z}_W \underline{I}_1}{2 \underline{Z}_W} \right) e^{\gamma x} \\ &= -\frac{\underline{V}_1}{\underline{Z}_W} \left( \frac{e^{\gamma x} - e^{-\gamma x}}{2} \right) + \left( \frac{e^{\gamma x} + e^{-\gamma x}}{2} \right) \underline{I}_1\end{aligned}$$

- We can recognise the hyperbolic functions cosh and sinh

$$\cosh(\gamma x) = \frac{e^{\gamma x} + e^{-\gamma x}}{2}, \quad \sinh(\gamma x) = \frac{e^{\gamma x} - e^{-\gamma x}}{2}$$

- Using cosh and sinh gives compact expressions, we obtain equations for propagation of voltage and current from beginning of line

$$\begin{aligned}\underline{V}(x) &= \cosh(\underline{\gamma}x)\underline{V}_1 - \underline{Z}_w \sinh(\underline{\gamma}x)\underline{I}_1 \\ \underline{I}(x) &= -\frac{\underline{V}_1}{\underline{Z}_w} \sinh(\underline{\gamma}x) + \cosh(\underline{\gamma}x)\underline{I}_1\end{aligned}$$

- In same way, we can define boundary conditions at end of line ( $x = \ell$ )


$$\underline{V}(\ell) = \underline{V}_2 \quad \underline{I}(\ell) = \underline{I}_2$$

and obtain equations for propagation of voltage and current from end of line

$$\begin{aligned}\underline{V}(x) &= \cosh(\underline{\gamma}(\ell - x))\underline{V}_2 + \underline{Z}_w \sinh(\underline{\gamma}(\ell - x))\underline{I}_2 \\ \underline{I}(x) &= \frac{\underline{V}_2}{\underline{Z}_w} \sinh(\underline{\gamma}(\ell - x)) + \cosh(\underline{\gamma}(\ell - x))\underline{I}_2\end{aligned}$$

- In practice, we often don't need to use the (rather complicated) wave equation to describe phenomena in power systems
  - Reason: Usually, we are interested in the voltage drop across a line or the reactive power flow, but not in the exact trajectory of the voltages and currents along the line
- Then, we may use simplified models for a power line without compromising the accuracy of our calculations too much
- We will discuss such models in the following
  - In particular, we will derive the  $\Pi$ -equivalent circuit of a transmission line

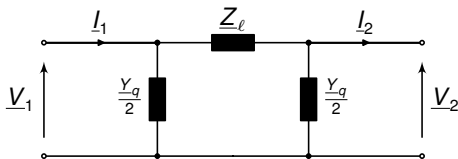
## 5.3 $\Pi$ -equivalent circuit of homogeneous power line (1)



- $\Pi$ -model contains lumped line parameters
- For model derivation, it is convenient to distribute shunt impedance  $\underline{Y}_q$  equally on both sides of quadrupole
- We will derive this model from the wave equation


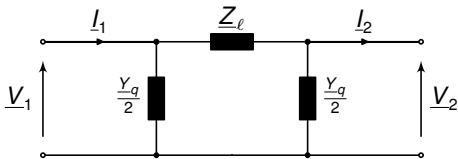
## 5.3 $\Pi$ -equivalent circuit of homogeneous power line (2)




- KCL and KVL yield

$$\begin{bmatrix} \underline{V}_1 \\ \underline{I}_1 \end{bmatrix} = \underbrace{\begin{bmatrix} 1 + \underline{Z}_\ell \frac{\underline{Y}_g}{2} & \underline{Z}_\ell \\ \frac{\underline{Y}_g}{2} \left( 2 + \underline{Z}_\ell \frac{\underline{Y}_g}{2} \right) & 1 + \underline{Z}_\ell \frac{\underline{Y}_g}{2} \end{bmatrix}}_{=A_1} \begin{bmatrix} \underline{V}_2 \\ \underline{I}_2 \end{bmatrix}$$

- From wave equation we obtain with  $\underline{V}_1 = \underline{V}(x=0)$  and  $\underline{I}_1 = \underline{I}(x=0)$
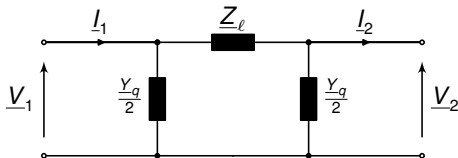
$$\begin{bmatrix} \underline{V}_1 \\ \underline{I}_1 \end{bmatrix} = \underbrace{\begin{bmatrix} \cosh(\underline{\gamma}\ell) & \underline{Z}_w \sinh(\underline{\gamma}\ell) \\ \frac{1}{\underline{Z}_w} \sinh(\underline{\gamma}\ell) & \cosh(\underline{\gamma}\ell) \end{bmatrix}}_{=A_2} \begin{bmatrix} \underline{V}_2 \\ \underline{I}_2 \end{bmatrix}$$




- Comparing coefficients of matrices  $A_1$  and  $A_2$  yields

$$\underline{Z}_\ell = \underline{Z}_W \sinh(\underline{\gamma}\ell)$$

$$\frac{\underline{Y}_q}{2} = \frac{\cosh(\underline{\gamma}\ell) - 1}{\underline{Z}_W \sinh(\underline{\gamma}\ell)} = \frac{1}{\underline{Z}_W} \tanh\left(\frac{\underline{\gamma}\ell}{2}\right)$$

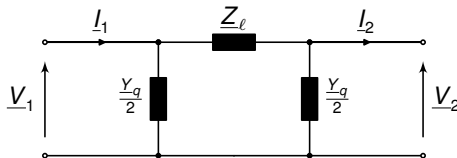- These parameters correspond to exact relations between currents and voltages according to wave equation for  $x = 0$  and  $x = \ell$



- For  $|\underline{\gamma}\ell| \ll 1$ , the expressions for  $\underline{Z}_\ell$  and  $\underline{Y}_q$  can be simplified

$$\underline{Z}_\ell = \underline{Z}_W \sinh(\underline{\gamma}\ell) \approx \underline{Z}_W \underline{\gamma}\ell = \underline{Z}'\ell$$

$$\frac{\underline{Y}_q}{2} = \frac{1}{\underline{Z}_W} \tanh\left(\frac{(\underline{\gamma}\ell)}{2}\right) \approx \frac{1}{\underline{Z}_W} \frac{\underline{\gamma}\ell}{2} = \frac{\underline{Y}'\ell}{2}$$

→ Concentrated elements  $\underline{Z}_\ell$  and  $\underline{Y}_q$  can be computed from *distributed* parameters  $R'$ ,  $L'$ ,  $G'$  and  $C'$  if  $|\underline{\gamma}\ell| \ll 1$

$$\boxed{\begin{aligned}\underline{Z}_\ell &= \underline{Z}'\ell = (R' + jX')\ell \\ \frac{\underline{Y}_q}{2} &= \frac{\underline{Y}'}{2}\ell = \frac{(G' + jB')}{2}\ell\end{aligned}}$$

- Accuracy of assumption  $|\underline{\gamma}\ell| \ll 1$  is crucial for validity of simplified equivalent  $\Pi$ -model
  - The larger  $|\underline{\gamma}\ell|$ , the worse the model with concentrated parameters  $\underline{Z}_\ell$  and  $\underline{Y}_q$  represents evolution of current and voltage along the line
- Whenever you use a simplified  $\Pi$ -model to represent a power line, be aware that the model accuracy reduces with increasing line length!
- Rule of thumb:
    - Max. length for overhead line  $\approx 300$  km
    - Max. length for cable  $\approx 100$  km
  - Therefore, long power lines are often split into several shorter sections in power flow calculations and each section is represented by individual (simplified)  $\Pi$ -model

**Task.** Consider a power line with the following characteristics

$$R' = 0.05 \, \Omega/\text{km}, \quad L' = 1.25 \, \text{mH}/\text{km}, \quad G' = 0 \, \mu\text{S}/\text{km}, \quad C' = 10 \, \text{nF}/\text{km}.$$

Suppose that the line length is 200 km and that the line is operated with a frequency of 50 Hz.

- 1) Calculate the series impedance  $\underline{Z}_\ell^E$  and the shunt admittance  $\underline{Y}_q^E$  for the exact  $\Pi$ -equivalent circuit.
- 2) If  $|\underline{\gamma}\ell| \ll 1$ , then calculate the simplified series impedance  $\underline{Z}_\ell$  and the shunt admittance  $\underline{Y}_q$  of the  $\Pi$ -equivalent circuit for that case.

## 5.3 Example: $\Pi$ -equivalent circuit of homogeneous power line (2)

**Solution.** (On board)

(On board)


---

<sup>3</sup>Physical explanation: We could model the considered line equivalently by two  $\Pi$ -equivalent circuits in series. Then, we would see that there are active power losses in the circuit. Thus, the single  $\Pi$ -equivalent circuit has to have an ohmic component.

## 5.3 Example: $\Pi$ -equivalent circuit of homogeneous power line (4)

(On board)



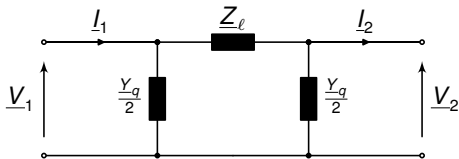


- In practice,  $G'$  is small (in particular for voltages  $\geq 110\text{kV}$ ) and therefore often neglected
- Then, shunt admittance is purely capacitive

$$\underline{Z}_\ell = \underline{Z}'\ell = (R' + jX')\ell \qquad \frac{Y_g}{2} = \frac{Y'}{2}\ell = \frac{jB'}{2}$$

- Some times, also conductor resistances neglected  $\rightarrow R' = 0$ ; such line model is called *lossless* and its concentrated (or lumped) parameters are given by


$$\underline{Z}_\ell = \underline{Z}'\ell = jX'\ell \qquad \frac{Y_g}{2} = \frac{Y'}{2}\ell = \frac{jB'}{2}\ell = \frac{j\omega C'}{2}\ell$$

- For *overhead lines* models can be further simplified
- Typically, overhead lines classified into 3 categories
  - **Short lines (up to 100 km).** Usually,  $C'$  and  $G'$  very small; model: series impedance  $\underline{Z}_\ell = R'\ell + j\omega L'\ell$ ; shunt admittance  $\underline{Y}_q$  is completely neglected
  - **Medium length lines (100 to 300 km).** Use of simplified  $\Pi$ -model with  $G' = 0$  without any significant loss of accuracy
  - **Long lines (larger than 300 km).** Significant inaccuracies with concentrated parameter model. Line should either be represented by wave equation or split into several shorter sections

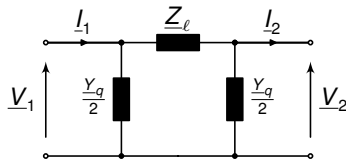

Medium length line model

$$\underline{Y}_q = jB'\ell$$

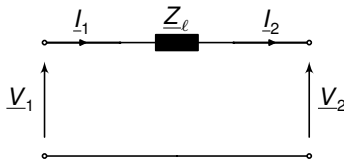

Short line model

$$\underline{Y}_q = 0$$

- We compare results obtained with different models for exemplary 230 kV transmission line with characteristic impedance and propagation constant

$$\underline{Z}_W = 382.2 - j16.5 \, \Omega \quad \underline{\gamma} = \alpha + j\beta = 0.0001 \, [\text{Np/km}] + j0.0011 \, [\text{rad/km}]$$

Np=Neper (logarithmic unit to measure physical field quantities)

- We seek to calculate voltage  $\underline{V}_2$  at end of line under *no load* conditions  
 $\rightarrow \underline{I}_2 = 0$
- We assume  $|\underline{V}_1| = 1.0 \, \text{pu}$
- We will explore 3 different ways
  - 1) Using the exact wave equation (Section 4.2)
  - 2) Using the medium length  $\Pi$ -equivalent circuit (Section 4.3)
  - 3) Using the short line model (Section 4.4)

- 1) For  $I_2 = 0$ , exact wave equation reduces to (see matrix  $A_2$ )

$$\underline{V}_1 = \underline{V}(x = 0) = \underline{V}_2 \cosh(\underline{\gamma}\ell)$$

- 2) Medium length  $\Pi$ -model

$$\underline{Z}_\ell \approx \underline{Z}_W \underline{\gamma}\ell \quad \frac{\underline{Y}_q}{2} \approx \frac{1}{\underline{Z}_W} \frac{\underline{\gamma}\ell}{2}$$

Hence,

$$\underline{V}_1 = \left(1 + \frac{\underline{Z}_\ell \underline{Y}_q}{2}\right) \underline{V}_2 = \left(1 + \frac{(\underline{\gamma}\ell)^2}{2}\right) \underline{V}_2$$


- 3) Short line model: there is no voltage drop across series element for zero current  $\rightarrow \underline{V}_2 = \underline{V}_1$

Values for  $|\underline{V}_2|$  obtained for different line lengths and different models

Length $\ell$ in km	$ \underline{\gamma}\ell $	1)	2)	3)
50	0.0552	1.0015	1.0015	1.000
100	0.1105	1.0060	1.0060	1.000
300	0.3314	1.0565	1.0570	1.000
500	0.5523	1.1710	1.1759	1.000

- For short line lengths ( $\leq 50$  km) all models provide almost identical results
- With increasing line length, results with short line clearly differ from those with other models
- Accuracy of  $\Pi$ -model fairly good up to 300 km, but increasing deviation with increasing length
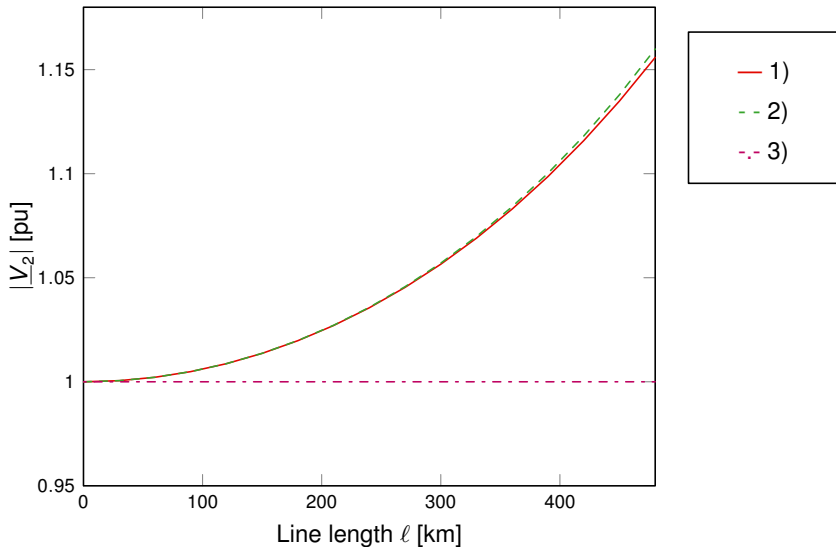
## 5.4 Model simplifications - Comparison: Plots



- Overhead lines most economic solution for long-distance power transmission
- An overhead line consists of conductors, support structures, shield wires and insulators
- Characteristics of power lines can be represented by set of concentrated parameters  $R'$ ,  $L'$ ,  $C'$  and  $G'$
- Exact propagation of voltage and current in a power line can be described by telegrapher's equations (in time-domain), respectively by the wave equation (in phasor-domain)
- For most practical applications, the use of a  $\Pi$ -equivalent circuit suffices to accurately describe the voltage and current relations on a power line
- The validity of the  $\Pi$ -model reduces significantly for long lines ( $>300$  km)